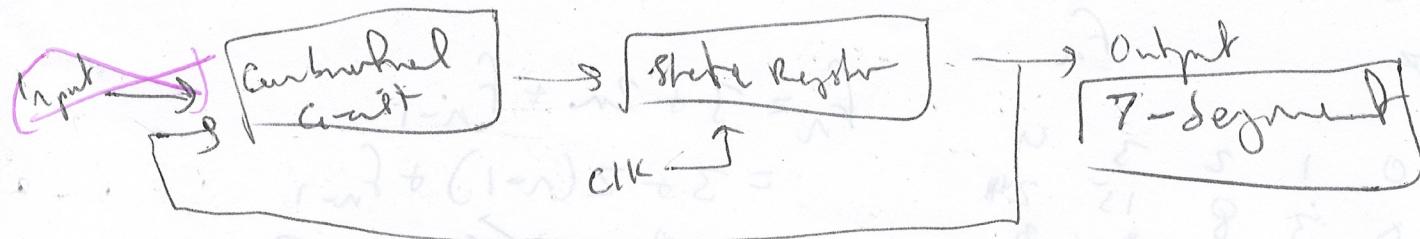


SYSL2310 - LAB 5: SEQUENTIAL LOGIC CIRCUITS


Esercizio 1: scrivere un programma

Name: Nani Zakkash
I.D.#:
ST#: (01143497)



State table:

State Diagram:

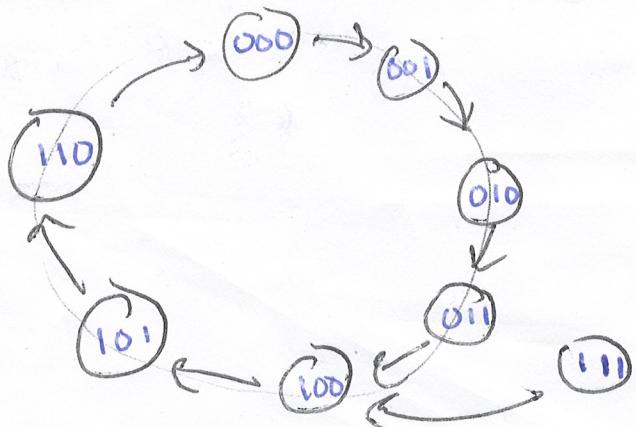


$$D_C = B^T C^T + A^T C^T$$

$$D_B = B^T C + A^T BC^T$$

Output C:

A	BC	00	01	11	10
0	-	-	-	-	C
1	i	-	-	X	-

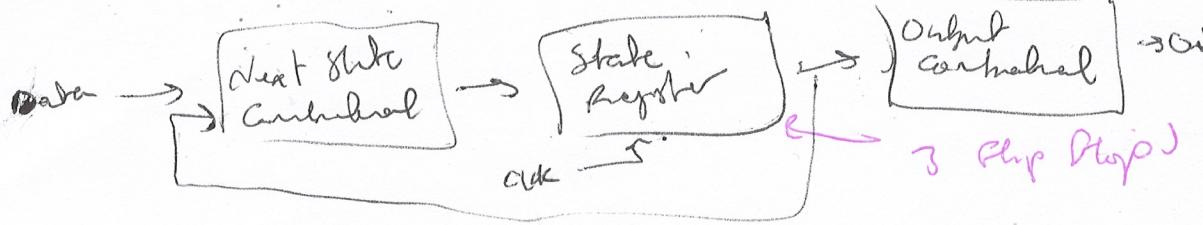Exercise 2: Design a Binary Sequence Detector



States:

State 000: done
 001: 1 detected
 010: 11 detected
 011: 110 detected
 100: 1101 detected

needed 1101

Present State	Input	next state			Output		
A	B	C	X	A'	B'	C'	y
0	0	0	0	0	0	0	0
0	0	0	1	0	0	1	0
0	0	1	0	0	0	0	0
0	0	1	1	0	1	0	0
0	1	0	0	0	1	1	0
0	1	0	1	0	1	0	0
0	1	1	0	0	0	0	0
0	1	1	1	1	0	0	1
1	0	0	0	0	0	0	0
1	0	0	1	0	1	0	0
1	0	1	0	X	X	X	0
1	0	1	1	X	X	X	0
1	1	0	0	X	X	X	0
1	1	0	1	X	X	X	0
1	1	1	0	X	X	X	0
1	1	1	1	X	X	X	0

Don't care
or
specify ???

Output A': pos

AB	00	01	11	10
Cx	00	00	00	00
AB	00	01	11	10
00	00	00	00	00
01	00	01	10	10
11	X	X	X	X
10	00	00	X	X

$$\begin{aligned}
 D_A &= (\bar{C})(\bar{x})(B) \\
 &= B \bar{C} \bar{x}
 \end{aligned}$$

Output B': pos

AB	00	01	11	10
Cx	00	01	11	10
AB	00	01	11	10
00	00	00	00	00
01	11	11	00	00
11	X	X	X	X
10	00	00	1X	X

$$D_B = (A + B + C)(B' + C')(x + B)$$

Exercise 2: Design a binary sequence detector (CONT)

Output C': P_{0,5}

A'B'C'	00 01 11 10
00 0 1 0 0	
01 1 0 0 0	
11 X X X X	
10 0 0 X X	

$$D_C = (A')(C')(B + X)(B' + X')$$

Output y: SOR


A'B'C'	00 01 11 10
00 0 1 0 0	
01 1 0 0 0	
11 X X X X	
10 0 0 X X	

$$y = A'B'C$$

$$(y = A'B'C)$$

State diagram:

- 8 total states
- 5 legitimate ones

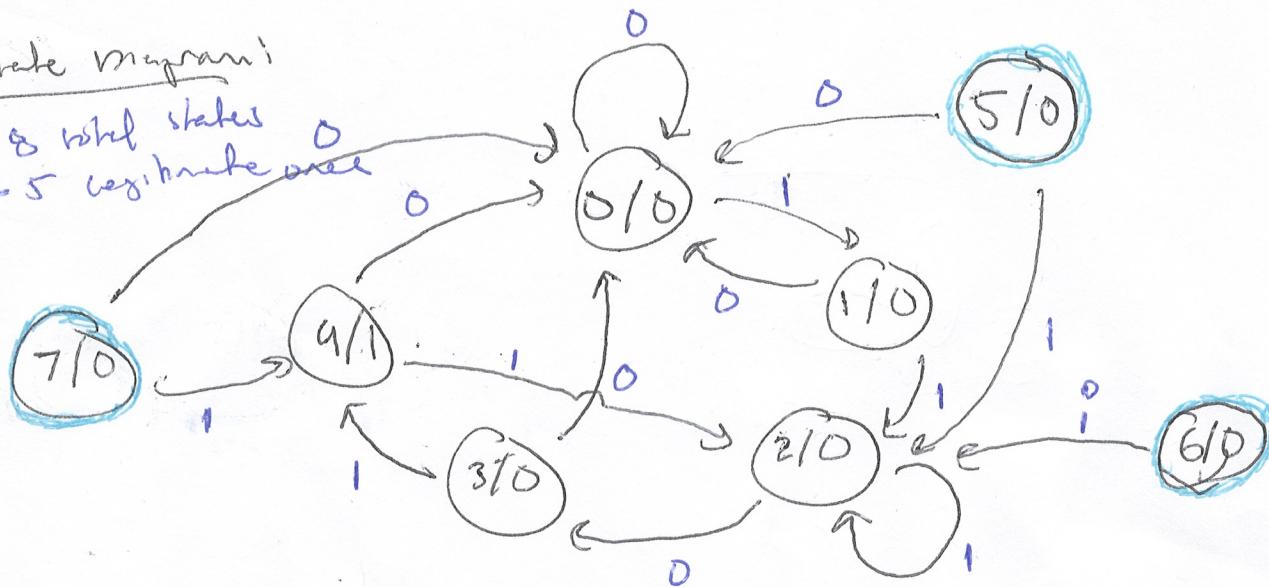

→ Note: the highlighted states should be impossible to enter and the only time they ever could is if the flip flops were manually adjusted to any of these states at startup.

Exercise 3: Design using a JK Flip Flop

JK Flip Flop Excitation Table:

$Q(t)$	$Q(t+1)$	J	K
0	0	0	X
0	1	1	X
1	0	X	1
1	1	X	0

Output

Present State A B C	Input X	next state A' B' C'	Flip Flop Inputs				Y
			J_A	K_A	J_B	K_B	
0 0 0	0	0 0 0	0	X	0	X	0
0 0 0	1	0 0 1	0	X	0	X	1
0 0 1	0	0 0 0	0	X	0	X	0
0 0 1	1	0 1 0	0	X	1	X	1
0 1 0	0	0 1 1	0	X	X	0	1
0 1 0	1	0 1 0	0	X	X	0	0
0 1 1	0	0 0 0	0	X	X	1	1
0 1 1	1	1 0 0	1	X	X	1	0
1 0 0	0	0 0 0	X	1	0	X	0
1 0 0	1	0 1 0	X	1	1	X	0
1 0 1	0	X X X	X	X	X	X	0
1 0 1	1	X X X	X	X	X	X	0
1 1 0	0	X X X	X	X	X	X	XX
1 1 0	1	X X X	X	X	X	X	XX
1 1 1	0	X X X	X	X	XX	XX	0
1 1 1	1	X X X	X	X	XX	XX	0

Output J_A :

Cx	00	01	11	10
AB	-	-	-	-
00	-	-	-	-
01	-	-	-	-
11	X	X	X	X
10	X	X	X	X

$$J_A = BCx$$

Output K_A :

Cx	00	01	11	10
AB	-	-	-	-
00	X	X	X	X
01	X	X	X	X
11	X	X	X	X
10	L	L	X	X

$$K_A = 1$$

Output J_B :

Cx	00	01	11	10
AB	-	-	-	-
00	0	0	1	0
01	X	X	X	X
11	X	X	X	X
10	0	1	X	X

$$J_B = Ax + Cx$$

Exercise 3 (contd) :

Output K_B:

AB\X	00	01	11	10
00	X	X	X	X
01	0	0	1	1
11	X	X	X	X
10	X	X	X	X

$$K_B = C$$

Output J_C:

AB\X	00	01	11	10
00	0	0	1	1
01	0	0	X	X
11	X	X	X	X
10	0	0	X	X

$$J_C = (B + X)(B' + X')(A')$$

Output K_C:

AB\X	00	01	11	10
00	X	X	1	1
01	X	X	1	1
11	X	X	X	X
10	X	X	X	X

$$K_C = 1$$

Output Y:

AB\BC	00	01	11	10
00	0	0	0	0
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$$y = A B' C'$$

COUNTING THE GATES:

D-Rippl Flops:

- 9 Gates used

JK Clip Flips:

- 9 Gates Used

Same number of gates used for both.