

STBC2310 Lab 3 - Exercise 1: PART 1A

= Four inputs, 2 outputs


- let A3, A2, A1, A0 be w, x, y, z respectively

P { true, number is PRIME
false, if not PRIME

D { true, if divisible by 3 or 4
false, " "

A3	A2	A1	A0	P	D
w	x	y	z		
0	0	0	1	0	0
0	0	1	0	1	0
0	0	1	1	1	1
0	1	0	0	0	1
0	1	0	1	1	0
0	1	1	0	0	1
0	1	1	1	1	0
1	0	0	0	0	1
1	0	0	1	0	1
1	0	1	0	0	0
1	0	1	1	1	0
1	1	0	0	0	1
1	1	0	1	1	0
1	1	1	0	0	0
1	1	1	1	0	1

Function P

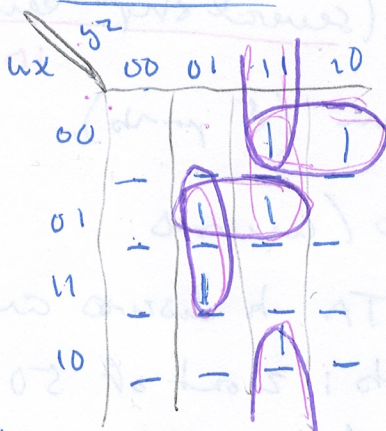


double pair
4 2-term implicants
↳ 4 3-terms
long SOP:

using POS:
- 2 terms
- 4 3-terms


$$P(w,x,y,z) = x'y'z + w'x'y + w'xz + xy'z$$

Function D

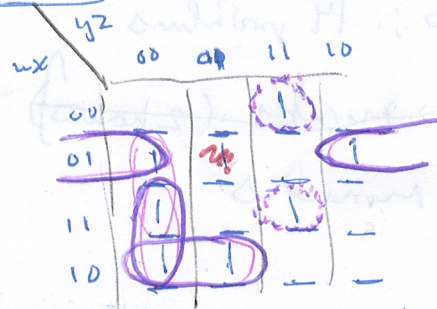

$$D(w,x,y,z) = w'xz + wx'y' + wy'z' + w'x'y'z + wxyz$$


Function P circuit

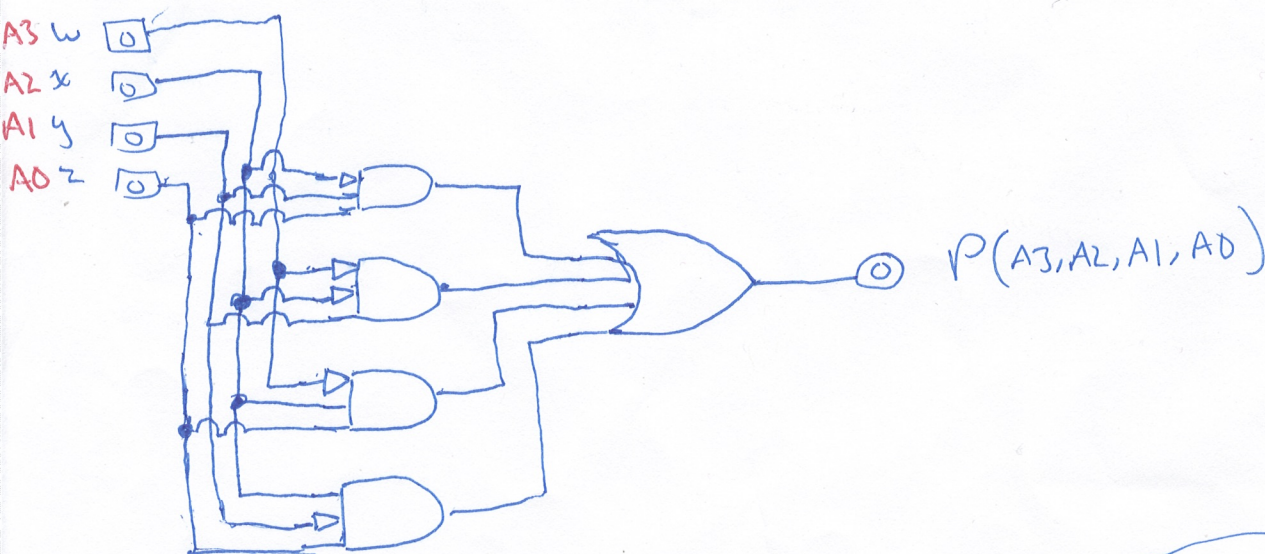


PART 1A

page 1

Function D diagram

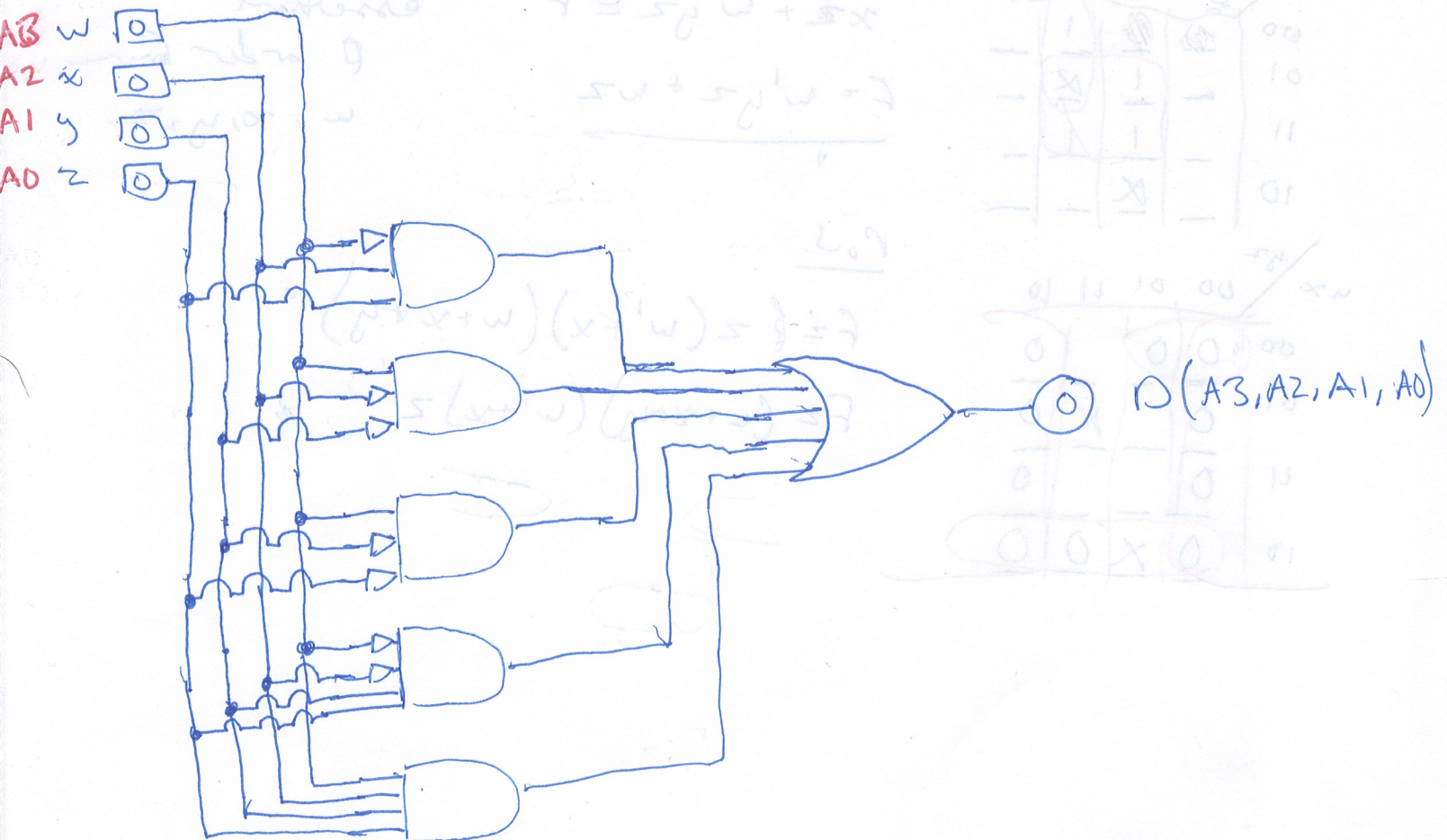

Main Diagram

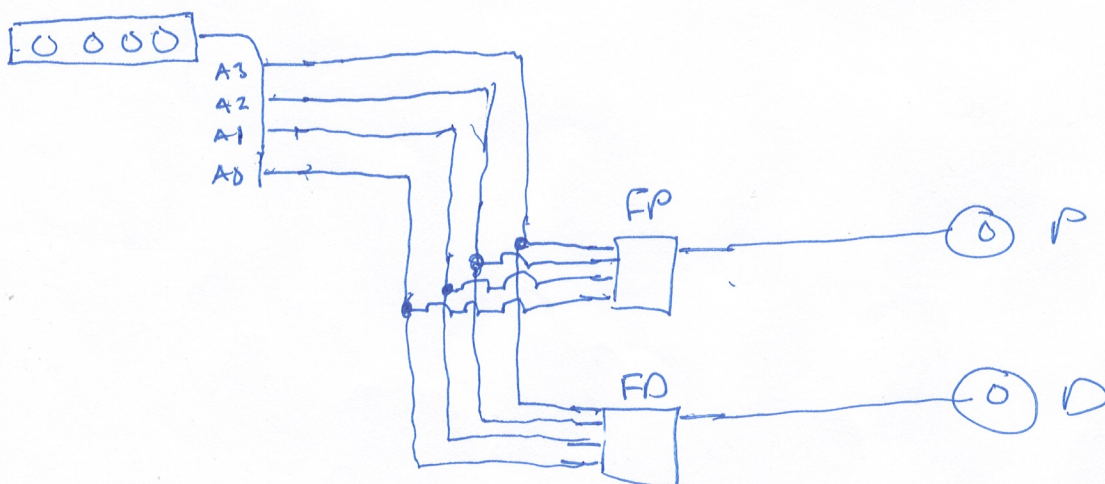

Counting the # of gates

3-input input AND: 7

4-input AND: 2

4-input OR: 1

5-input OR: 1

A	B	C	D	E
1	0	1	0	0
0	1	0	1	1

Two labels later
Not whether

$$f(A, B, C) = A'B'C + A'B'C' + A'BC + A'BC'$$

The goal of the K-map, then is to find the simplest expression for the function.

$$f(A, B, C) = A \oplus B \oplus C$$

Given expression:

Find X:

