

SYSC2310 – LAB 2 REPORT**1.0 EXERCISE 1: SIMPLIFY A BOOLEAN LOGIC FUNCTION****1.1 Description of Circuit's Operation**

In Exercise 1, students were required to build a digital circuit representing the equation seen in Figure 1, labelled Function 1 (F1), and were then required to build an equivalent simplified circuit consisting of a max of 5 literals, shown in Figure 2, labelled Function 2 (F2).

$$F_1 = xy'z + x'y'z + w'xy + wx'y + wxy$$

Figure 1. Equation representing Function 1 in Exercise 1

$$F_2 = y'z + yx + yw$$

Figure 2. Equation representing Function 2 in Exercise 1

Boolean logical equivalence rules were used to derive Function 2 from Function 1. The digital circuit diagrams for Function 1 and Function are shown in Figure 3 and in Figure 4, respectively.

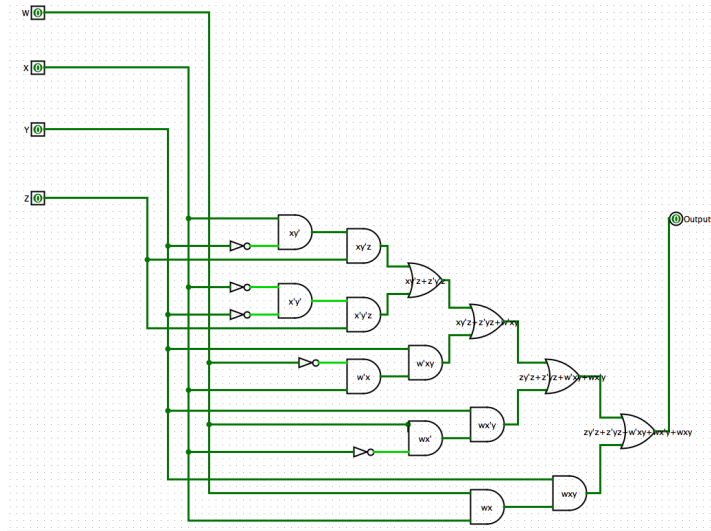


Figure 3. Screenshot of Function 1 circuit in Exercise 1

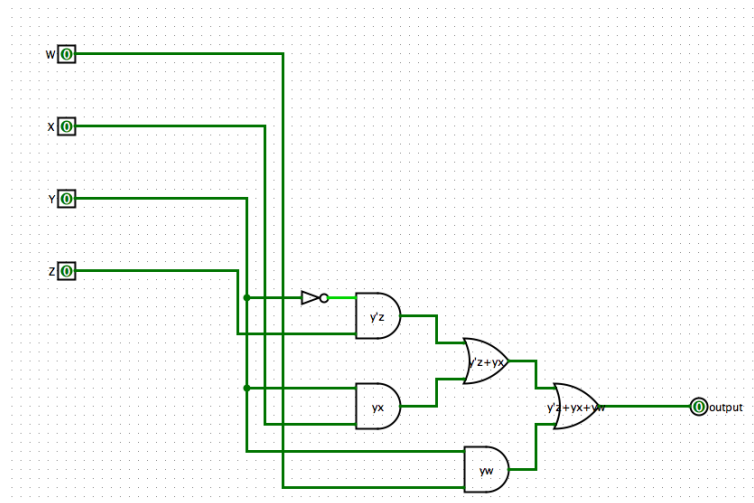


Figure 4. Screenshot of Function 2 circuit in Exercise 1

1.2 Verifying the Circuit's Operation

To prove that Function 1 and Function 2 were equivalent, the outputs of the two functions were inputted into an XNOR gate, which produces a '1' if the inputs are equal and a '0' if the inputs

are different, as seen in Figure 5.

 


Figure 5. Screenshot of circuit comparing the equivalence of Function 1 and Function 2 in

Exercise 1

2.0 EXERCISE 2: CONVERT A SET OF BOOLEAN FUNCTIONS TO A CIRCUIT

2.1 Description of Circuit's Operation

The circuit built in Exercise 2 performed 2-bit by 2-bit binary multiplication operation, shown in Figure 6. The circuit was designed using the functions shown in Figure 7 and were individually built as subcircuits and implemented together. The diagrams for M_0 , M_1 , M_2 , and M_3 are found in Figures 8, 9, 10, and 11, respectively.

 


Figure 6. 2-bit by 2-bit binary multiplication circuit in Exercise 2

$$M_0 = A_0 B_0$$

$$M_1 = A_0 B_1 \oplus A_1 B_0$$

$$M_2 = (A_0 B_1 * A_1 B_0) \oplus A_1 B_1$$

$$M_3 = A_0 B_1 * A_1 B_0 * A_1 B_1$$

Figure 7. Functions implemented in 2-bit by 2-bit binary multiplication digital circuit in Exercise 2

 


Figure 8. Subcircuit diagram for M_0 in Exercise 2

 


Figure 9. Subcircuit diagram for M_1 in Exercise 2

 


Figure 10. Subcircuit diagram for M_2 in Exercise 2

 


Figure 11. Subcircuit diagram for M_3 in Exercise 2

2.2 Verification of Circuit's Operation

The circuit's operation was verified through the use of log sheets, as shown in Figure 12. Since the circuit is a 2-bit by 2-bit multiplier, the range of the inputs are from 0 to 3, and the range of the outputs are from 0 to 9.

Logisim: Log main of Ex2

Selection Table File

A	B	Output(800,370)
0	0	0
1	0	0
3	0	0
3	1	3
3	3	9
3	1	3
3	3	9
3	3	9
1	3	3
3	3	9
2	3	6
2	1	2
2	0	0
2	2	4
0	2	0
1	2	2
3	2	6

Close Window

Figure 12. Screenshot log sheet in Exercise 2

3.0 EXERCISE 3: DESIGN A 3-BIT BY 2-BIT BINARY MULTIPLIER

3.1 Description of Circuit's Operation

The circuit in Exercise 3 performs a 3-bit by 2-bit multiplication operation and the diagram is shown in Figure 13. The circuit utilizes the half-adder and full-adder from Lab 1. The equation was derived using the procedure for multiplying two binary numbers and combines inputs into the half- and full-adders and is found for this circuit in Figure 14. The 6 subcircuits in column use an AND gate on two inputs, seen in Figure 15. The half-adder and full-adder diagrams are

shown in Figures 16 and 17, respectively.

 


Figure 13. Screenshot of 3-bit by 2-bit multiplication circuit diagram in Exercise 3

$$M_0 = A_0B_0$$

$$M_1 = A_0B_1 \oplus A_1B_0$$

$$M_3 = A_2B_1 \oplus (A_1B_1A_2B_0 + A_0B_1A_1B_0(A_1B_1 \oplus A_2B_0))$$

$$M_4 = A_2B_1(A_1B_1A_2B_0 + A_0B_1A_1B_0(A_1B_1 \oplus A_2B_0))$$

Figure 14. Equations derived for the solution of a 3-bit by 2-bit binary multiplication operation

 


Figure 15. AND operation for two inputs in Exercise 3

 


Figure 16. Half-adder circuit from Lab 1, used in Exercise 3


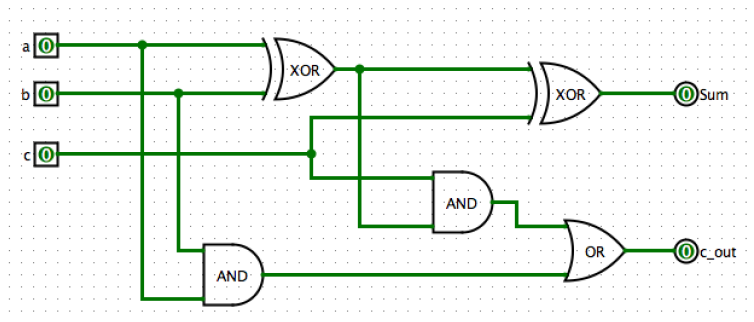


Figure 17. Full-adder circuit from Lab 1, used in Exercise 3.

 3.2 Verification of Circuit's Operation

The circuit's operation was verified using Logisim's logging feature, seen in Figure 18. Since the circuit is a 3-bit by 2-bit multiplier, the range of the outputs is between 0 and 21.



The screenshot shows a window titled "Logisim: Log main of Ex3". It has three tabs: "Selection", "Table", and "File". The "Table" tab is active, displaying a table with three columns: A, B, and M. The table contains 16 rows of data. At the bottom of the window is a "Close Window" button.

A	B	M
0	0	0
2	0	0
3	0	0
3	2	6
3	3	9
3	1	3
7	1	7
5	1	5
5	3	15
5	2	10
4	2	8
6	2	12
6	0	0
7	0	0
7	2	14
7	3	21

Figure 18. Screenshot of Logisim log