

INTRODUCTION TO DIGITAL SYSTEMS

SYSC2310 (Fall 2020)

Dr. Mostafa Taha

Lab 3: Answer Sheet

Exercise 1: Design an Arbitrary Function.

$$P = \overline{A_2} A_1 A_0 + \overline{A_3} \overline{A_2} A_1 + \overline{A_3} A_2 A_0 + A_2 \overline{A_1} A_0$$

$$D = \overline{A_3} A_2 A_0 + A_3 \overline{A_2} \overline{A_1} + A_3 \overline{A_1} \overline{A_0} + \overline{A_3} \overline{A_2} A_1 A_0 + A_3 A_2 A_1 A_0$$

The total number of AND and OR gates is:

3-pin AND: 7 4-pin AND: 2 4-pin OR: 1 5-pin OR: 1

Exercise 2: BCD to 7-Segment Decoder (IC 7447)

$$S_a = \overline{D_2} \overline{D_0} + D_3 + D_1 + D_2 D_0$$

$$S_b = \overline{D_2} + \overline{D_1} \overline{D_0} + D_1 D_0$$

$$S_c = \overline{D_1} + D_0 + D_2$$

$$S_d = \overline{D_2} D_0 + \overline{D_2} D_1 + D_1 \overline{D_0} + D_3 + D_2 \overline{D_1} D_0$$

$$S_e = \overline{D_0} (\overline{D_2} + D_1)$$

$$S_f = \overline{D_1} \overline{D_0} + D_2 \overline{D_0} + D_2 \overline{D_1} + D_3$$

$$S_g = D_2 \overline{D_1} + D_3 + \overline{D_2} D_1 + D_1 \overline{D_0}$$

The total number of AND and OR gates is:

2-pin AND: 14 3-pin AND: 1 4-pin OR: 3 3-pin OR: 2 5-pin OR: 1 2-pin OR: 1